
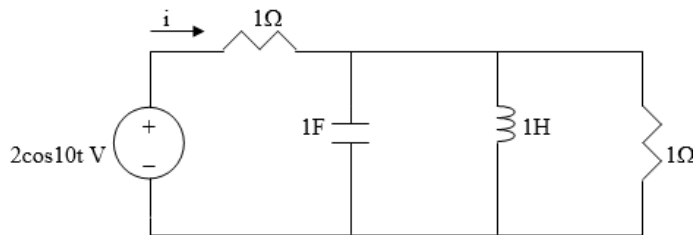


HW 10_Ch10

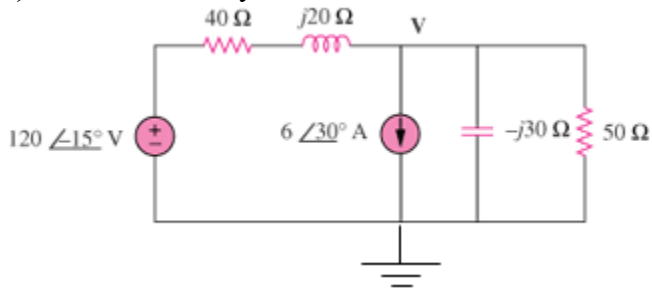
1) Determine $i(t)$ in the circuit below.




2) Use nodal analysis to find V in the circuit below.



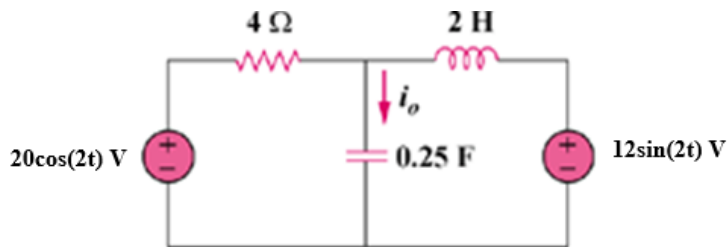
3) Solve for i_o in the circuit below using mesh analysis.



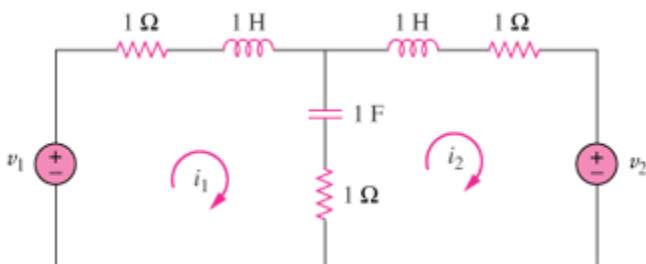
4) In the circuit below, determine the mesh currents i_1 and i_2 . Let $v_1 = 10 \cos 4t \text{ V}$ and $v_2 = 20 \cos(4t - 30^\circ) \text{ V}$.



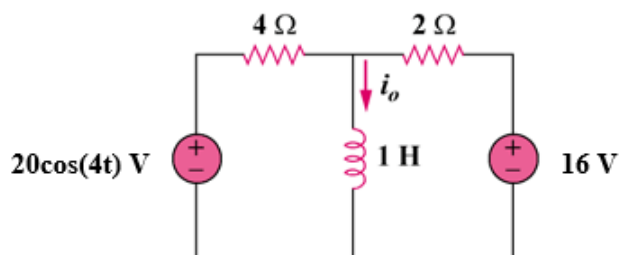
5) Find i_o in the circuit below using superposition.




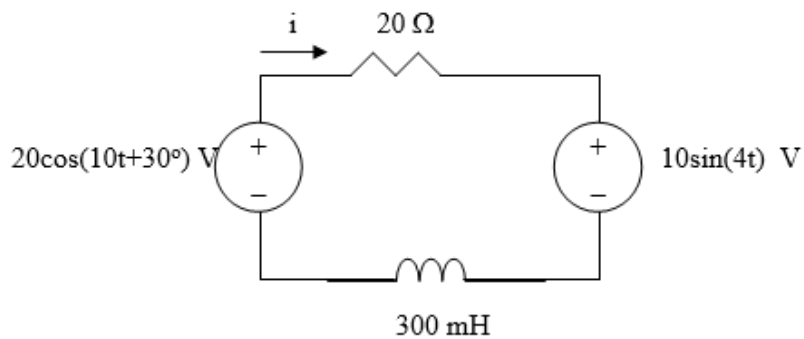
6) Use superposition to find $i(t)$ in the circuit below.



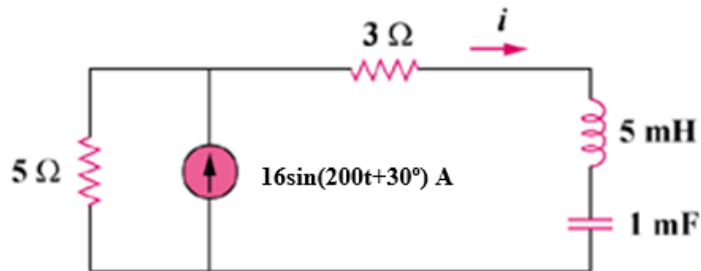
7) Using source transformation, find i in the circuit below.



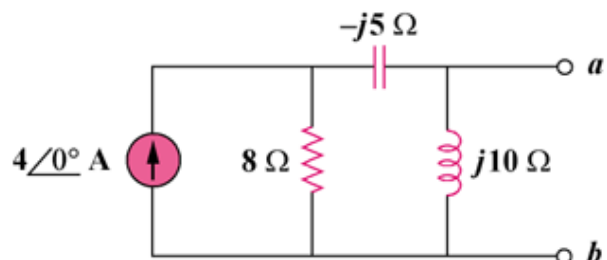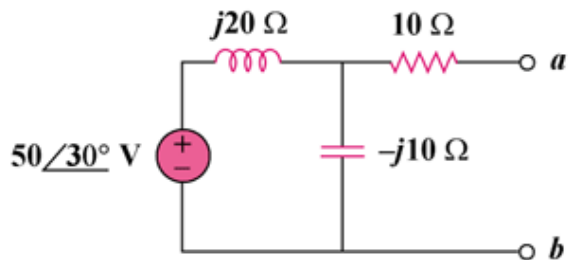8) Find the Thevenin and Norton equivalent circuits at terminals $a-b$ for each of the circuits below.



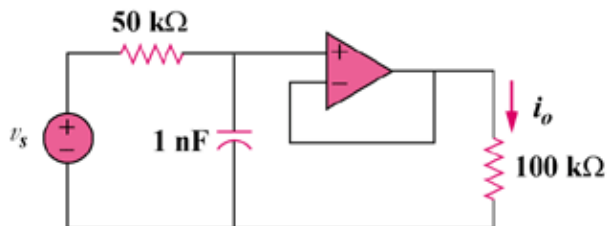9) Compute $i_o(t)$ in the op amp circuit below if $v_s = 10 \cos(10^4 t + 30^\circ)$ V.



10) For the op amp circuit below, obtain $v_o(t)$.

