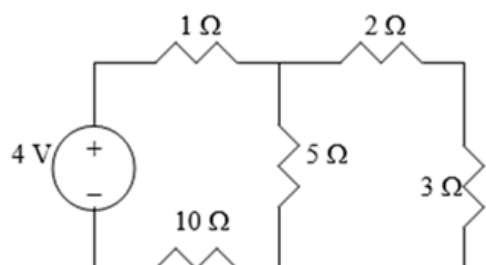



ENGR 2303: Electrical Science

HW 2_Ch2

1) Find the number of branches and nodes in each of the circuits below




(a)

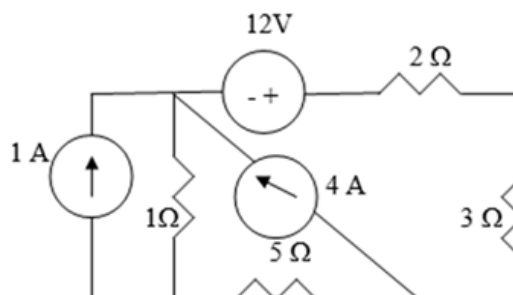


(b)


2) Find i_1 , i_2 , and i_3

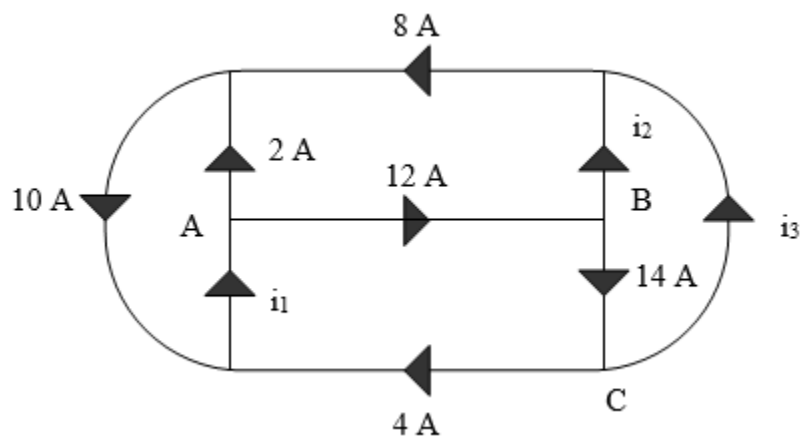

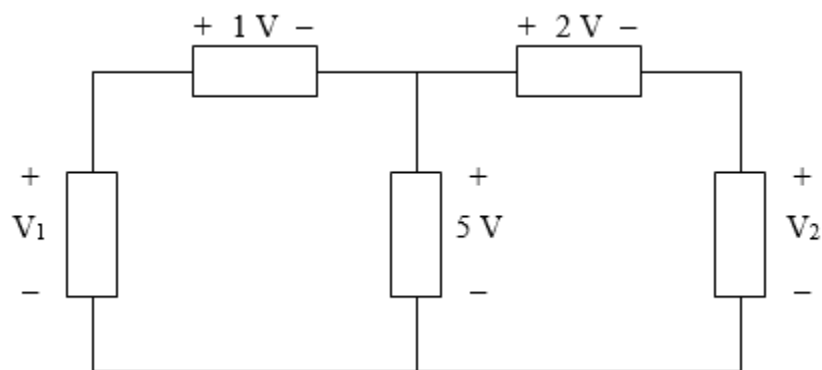
3) In the circuit below, calculate V_1 and V_2 .



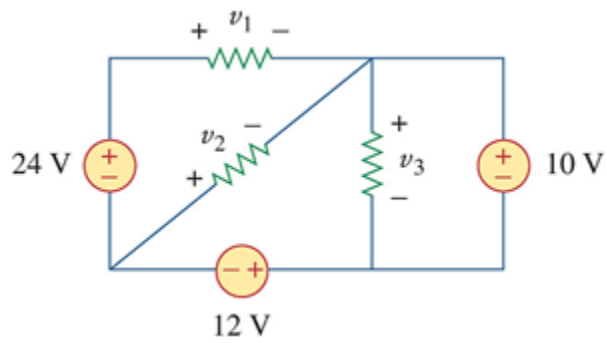
4) Obtain v_1 , v_2 , and v_3 in the circuit below




5) Find V_x in the circuit below

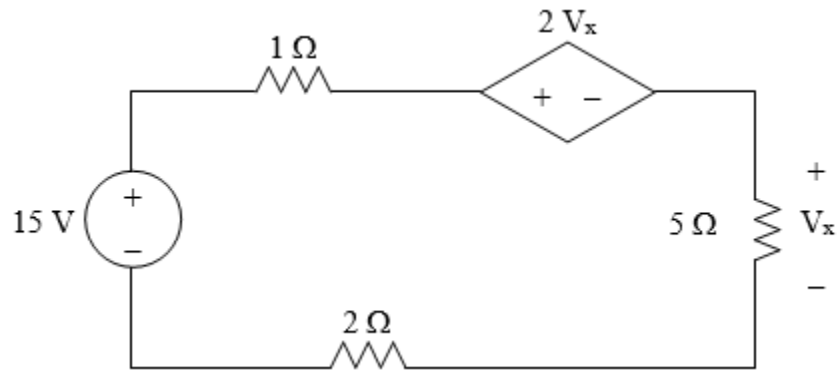

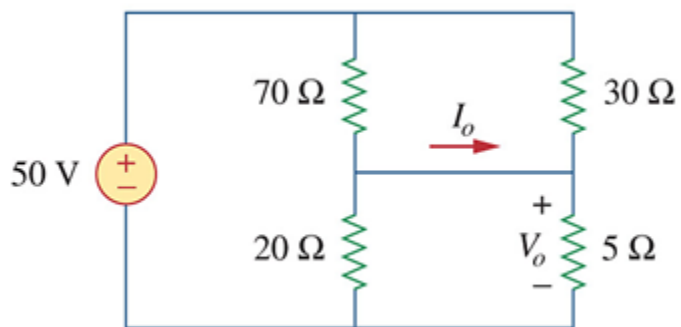
6) Calculate V_o and I_o in the circuit below



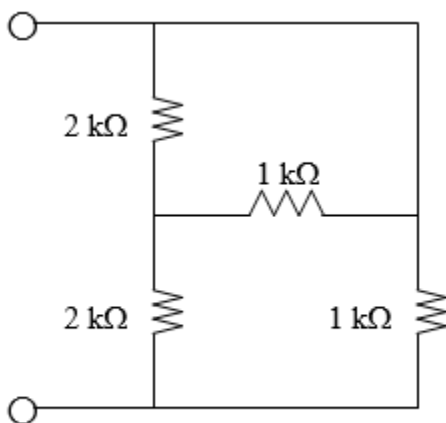7) Evaluate R_{eq} for each of the circuits shown below



(a)

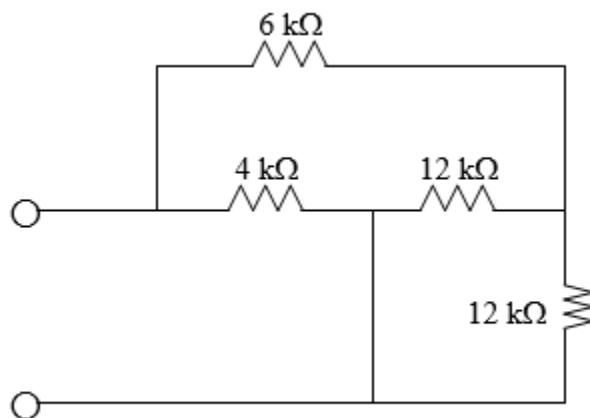

(b)


- 8) As a design engineer, you are asked to design a lighting system consisting of a 70-W power supply and two lightbulbs as shown in figure below. You must select the two bulbs from the following three available bulbs.

$$R_1 = 80\Omega, \text{ cost} = \$0.60 \text{ (standard size)}$$

$$R_2 = 90\Omega, \text{ cost} = \$0.90 \text{ (standard size)}$$

$$R_3 = 100\Omega, \text{ cost} = \$0.75 \text{ (nonstandard size)}$$

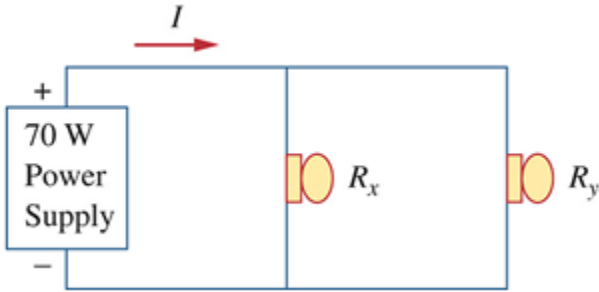The system should be designed for minimum cost such that $I = 1.2\text{ A} \pm 5\text{ percent}$.



- 9) Two delicate devices are rated as shown in figure below. Find the values of the resistors R_1 and R_2 needed to power the devices using a 24-V battery.

