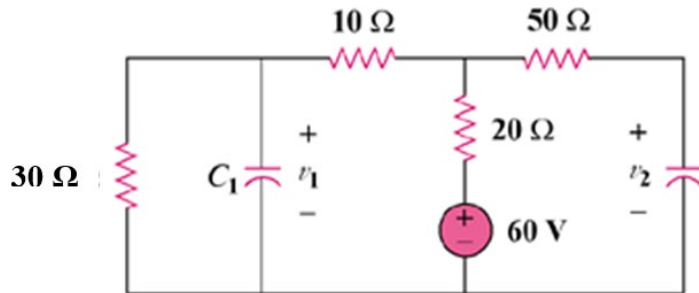


ENGR 2303: Electrical Science


HW 6_Ch6

- 1) The current through a 0.5-F capacitor is $6(1-e^{-t})$ A. Determine the voltage and power at $t=2$ s. Assume $v(0) = 0$.


- 2) Find the voltage across the capacitors in the circuit below under dc conditions.



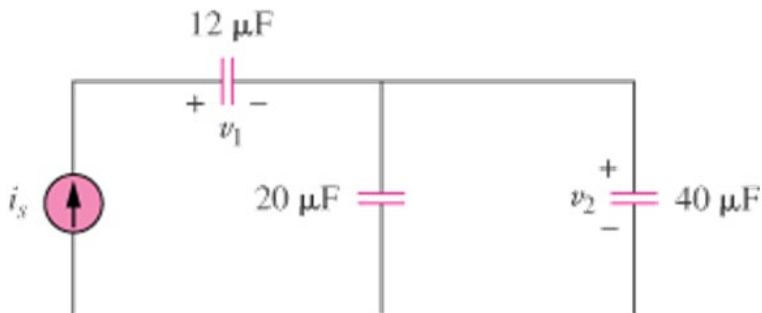
- 3) In the circuit below, let $i_s = 30e^{-2t}$ mA and $v_1(0) = 50$ V, $v_2(0) = 20$ V. Determine: (a) $v_1(t)$ and $v_2(t)$, (b) the energy in each capacitor at $t = 0.5$ s.



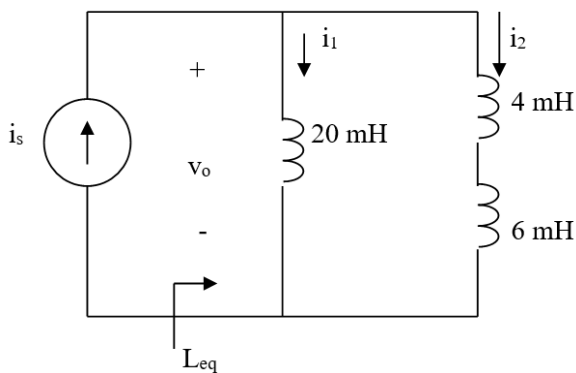- 4) Consider the circuit below. Find: (a) L_{eq} , $i_1(t)$ and $i_2(t)$ if $i_s = 3e^{-t}$ mA, (b) $v_o(t)$, (c) energy stored in the 20-mH inductor at $t=1$ s.



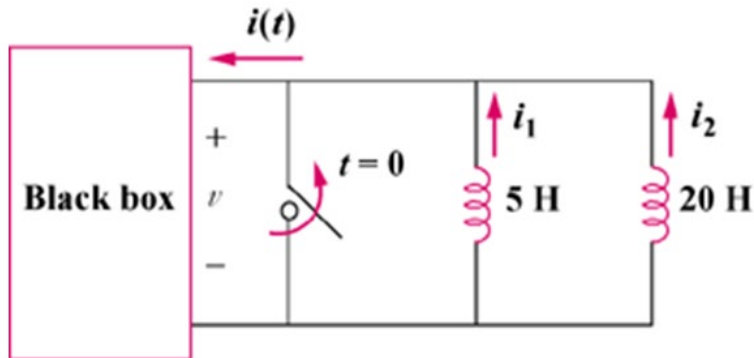- 5) The inductors in the circuit below are initially charged and are connected to the black box at $t = 0$. If $i_1(0) = 4$ A, $i_2(0) = -2$ A, and $v(t) = 50e^{-200t}$ mV, $t \geq 0$ find:
- the energy initially stored in each inductor,
 - the total energy delivered to the black box from $t = 0$ to $t = \infty$,
 - $i_1(t)$ and $i_2(t)$, $t \geq 0$,
 - $i(t)$, $t \geq 0$.



- 6) An op amp differentiator has $R = 250\text{ k}\Omega$ and $C = 10\text{ }\mu\text{F}$.

The input voltage is a ramp $r(t) = 12t$ mV. Find the output voltage.

- 7) Design an analog computer circuit to solve the following ordinary differential equation.

$$\frac{dy(t)}{dt} + 4y(t) = f(t) \quad \text{where } y(0) = 1\text{ V.}$$