

# Capacitors and Inductors

## Video 10

### Electrical Science

Dr. Mohamed Bingabr


University of Central Oklahoma

# Capacitors and Inductors


- Capacitors
- Series and Parallel Capacitors
- Inductors
- Series and Parallel Inductors
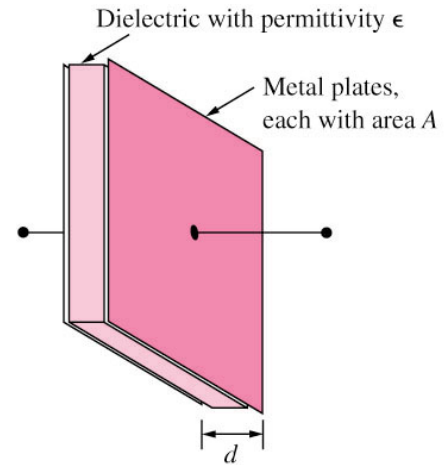
# Capacitors

- A **capacitor** consists of two conducting plates separated by an insulator (or dielectric).
- Where  $\epsilon$  is the permittivity of the dielectric material between the plates,  $A$  is the surface area of each plate,  $d$  is the distance between the plates.
- A capacitor is a passive element designed to **store energy** in its **electric field**.
- **Capacitance**  $C$  is the ratio of the charge  $q$  on one plate of a capacitor to the voltage difference  $v$  between the two plates, measured in farads (F).



$$C = \frac{\epsilon A}{d}$$

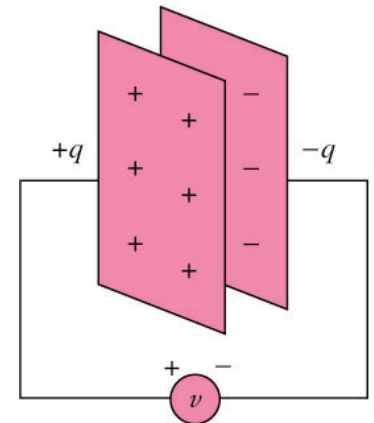


$$C = q/v$$

3
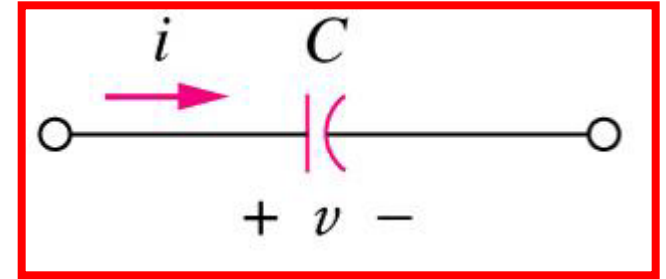
# Capacitor Current and Voltage

- If  $i$  is flowing into the +ve terminal of C

- Charging  $\Rightarrow i$  is +ve
- Discharging  $\Rightarrow i$  is -ve



- The current-voltage relationship of capacitor

$$i = C \frac{d v}{d t}$$

$$v = \frac{1}{C} \int_{t_0}^t i d t + v(t_0)$$

- The energy stored in the capacitor is


$$w = \frac{1}{2} C v^2$$

- A capacitor is an **open circuit** to dc ( $dv/dt = 0$ ).

# Capacitors
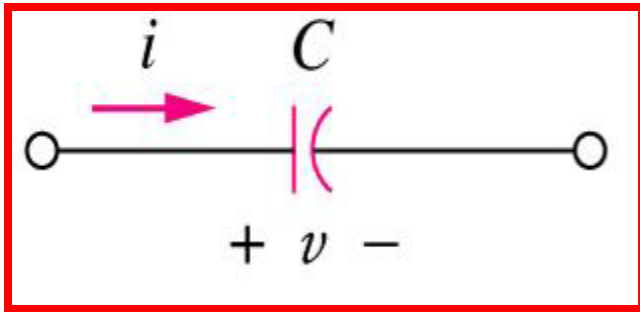
## Example 1

The current through a  $100\text{-}\mu\text{F}$  capacitor is  $i(t) = 50 \sin(120\pi t)$  mA. Calculate the voltage across it at  $t = 1$  ms and  $t = 5$  ms. Take  $v(0) = 0$ .




**Answer:  $v(1\text{ms}) = 93.14\text{mV}$      $v(5\text{ms}) = 1.7361\text{V}$**

# Capacitors
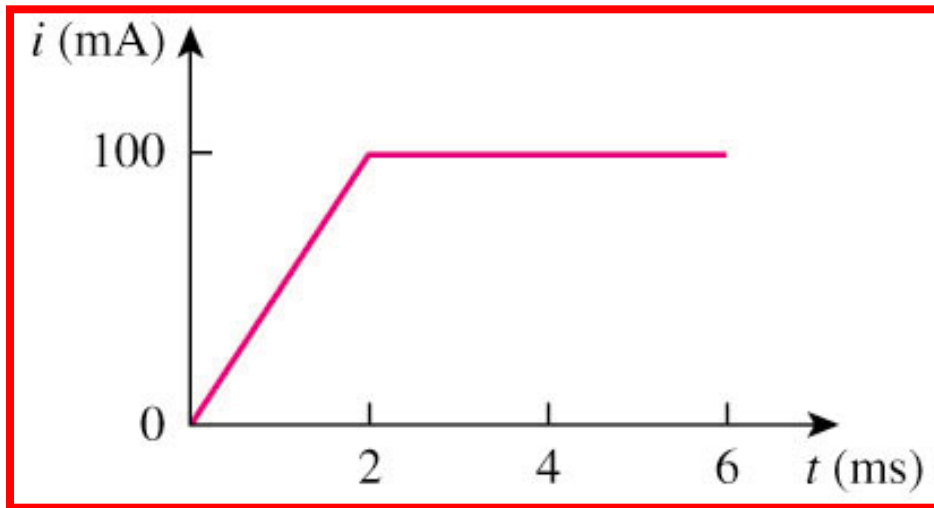
## Example 2


An initially uncharged 1-mF capacitor has the current shown below across it. Calculate the voltage across it at  $t = 2$  ms and  $t = 5$  ms.



**Answer:  $v(2\text{ms}) = 100$  mV  $v(5\text{ms}) = 400$  mV**

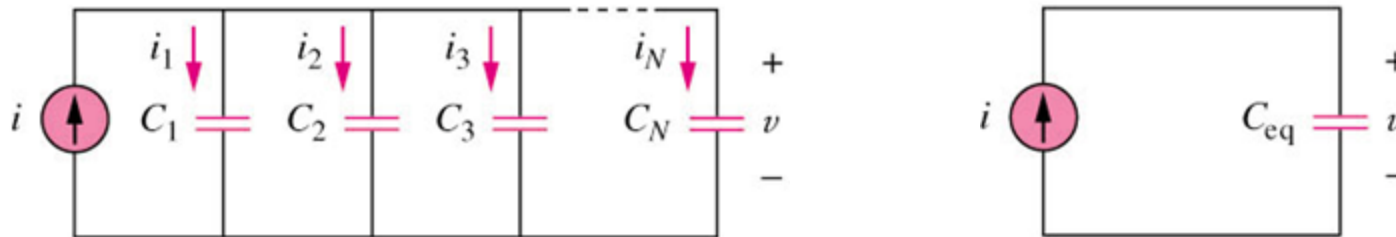
# Parallel Capacitors

- The equivalent capacitance of  $N$  **parallel-connected** capacitors is the sum of the individual capacitances.



$$C_{eq} = C_1 + C_2 + \dots + C_N$$

- Current Divider Rule

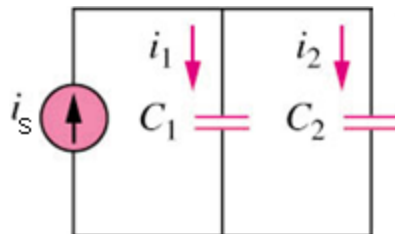


$$i_1 = \frac{C_1}{C_1 + C_2} i_s$$


$$i_2 = \frac{C_2}{C_1 + C_2} i_s$$
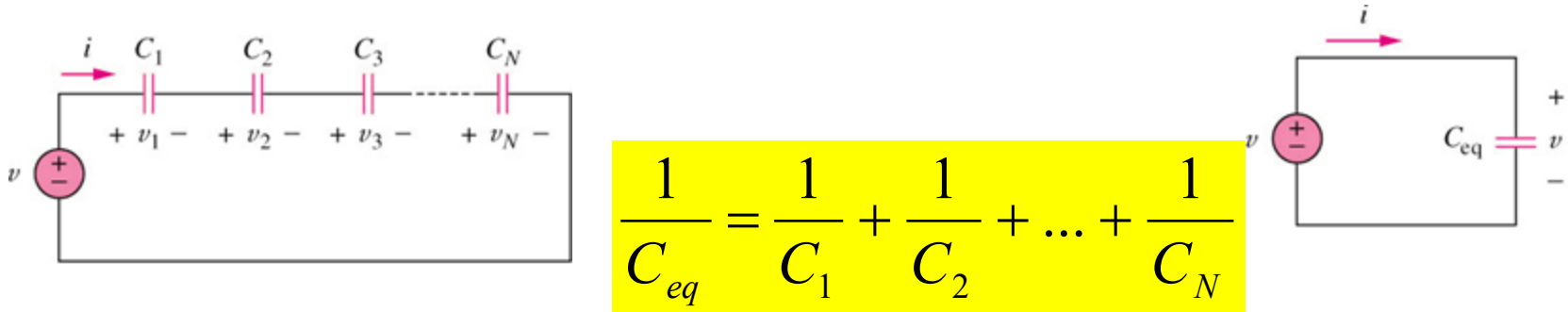
# Series Capacitors

- The equivalent capacitance of  $N$  **series-connected** capacitors is the reciprocal of the sum of the reciprocals of the individual capacitances.



- Voltage Divider Rule

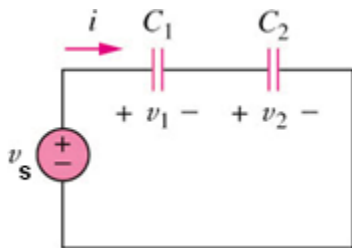

$$v_1 = \frac{C_2}{C_1 + C_2} v_s$$


$$v_2 = \frac{C_1}{C_1 + C_2} v_s$$



# Series and Parallel Capacitors
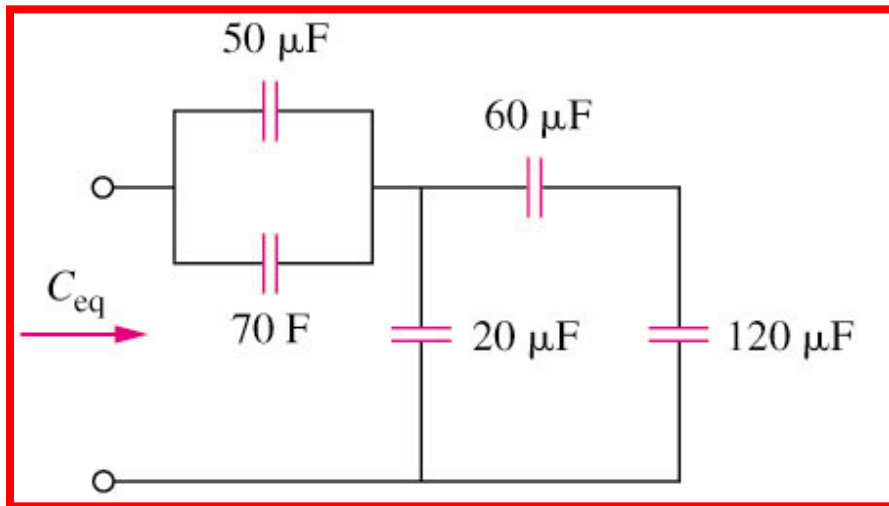
## Example 3

Find the equivalent capacitance seen at the terminals of the circuit in the circuit shown below:




**Answer:  $C_{eq} = \underline{40\ \mu\text{F}}$**

# Series and Parallel Capacitors
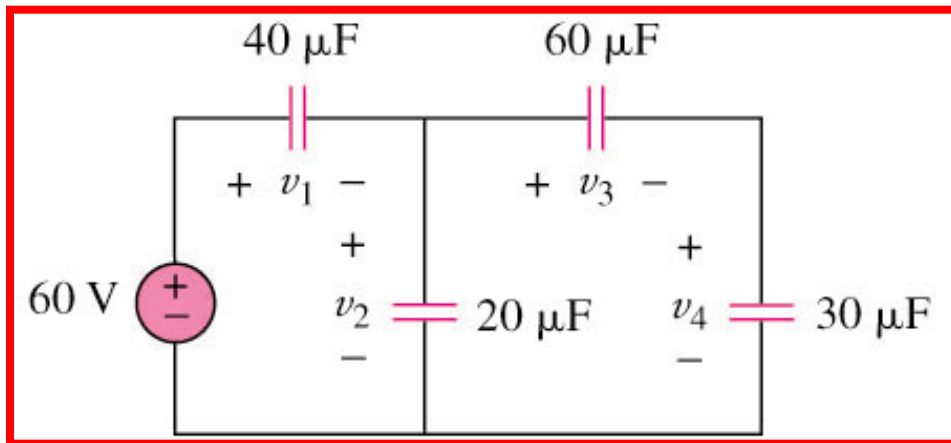
## Example 4


Find the voltage across each of the capacitors in the circuit shown below:



**Answer:  $v_1 = 30\text{V}$   $v_2 = 30\text{V}$   $v_3 = 10\text{V}$   $v_4 = 20\text{V}$**
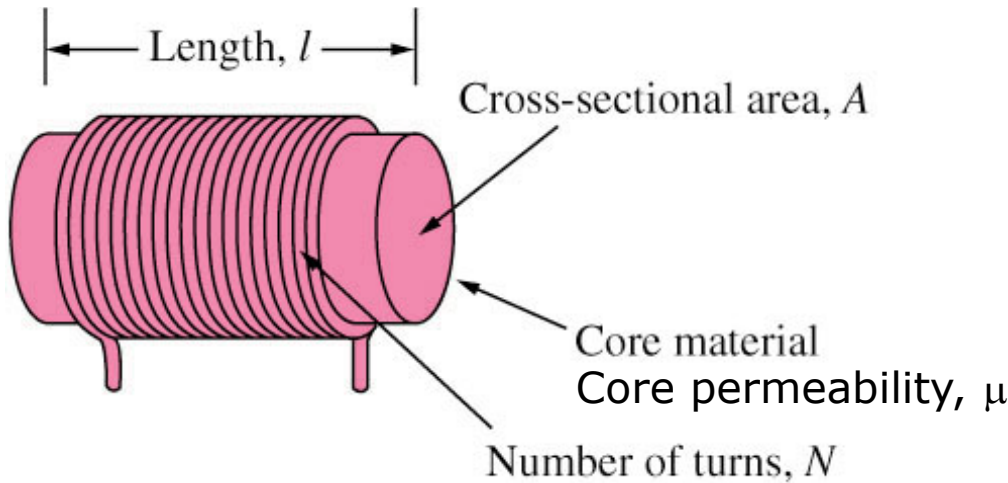
# Inductors

- An inductor is a passive element designed to store energy in its magnetic field.
- An inductor consists of a coil of conducting wire.



$$L = \frac{N^2 \mu A}{l}$$

$$v = L \frac{di}{dt}$$

- Inductance is the property whereby an inductor exhibits opposition to the change of current flowing through it, measured in henrys (H).
- An inductor acts like a short circuit to dc ( $di/dt = 0$ ) and its current cannot change abruptly.


# Inductors Voltage and Current

- The current-voltage relationship of an inductor:

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

- The energy stored by an inductor:


$$w = \frac{1}{2} L i^2$$

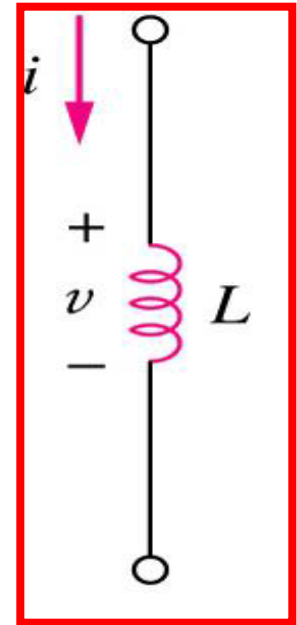

# Inductors
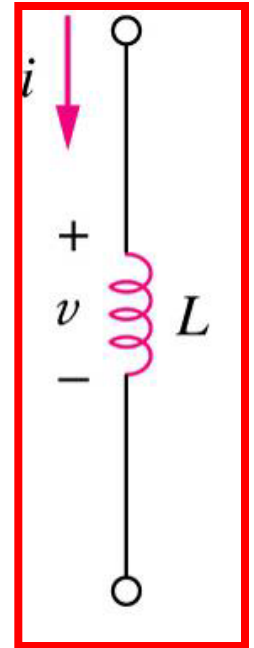
## Example 5

The terminal voltage of a 2-H inductor is  $v = 10(1-t)$  V  
Find the current flowing through it at  $t = 4$  s and the energy stored in it within  $0 < t < 4$  s. Assume  $i(0) = 2$  A.




**Answer:  $i(4s) = -18A$     $w(4s) = 320J$**

# Inductors
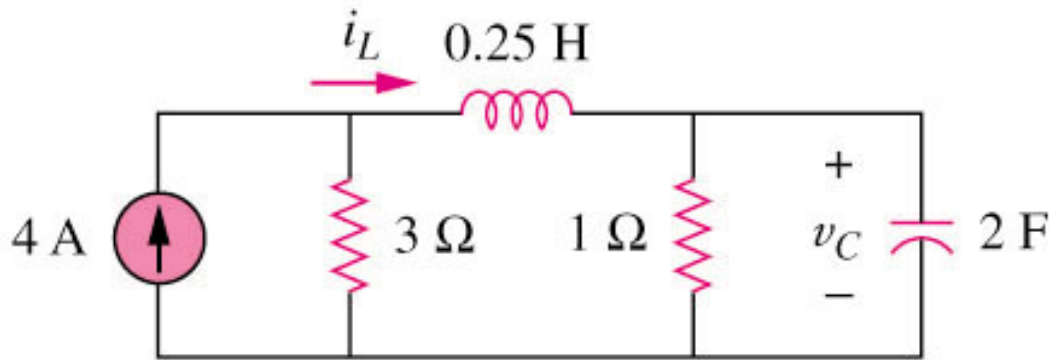
## Example 6



Determine  $v_C$ ,  $i_L$ , and the energy stored in the capacitor and inductor in the circuit shown below under dc conditions.



**Answer:  $i_L = 3A$     $v_C = 3V$     $w_L = 1.125J$     $w_C = 9J$**

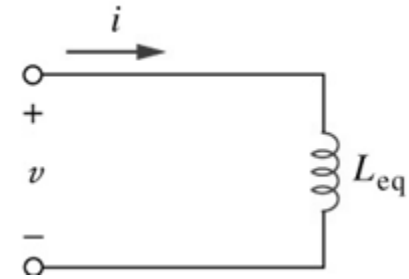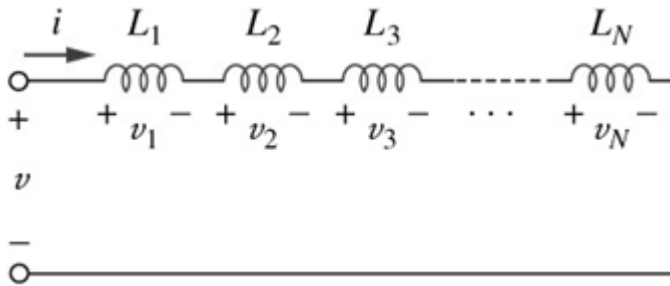
# Series Inductors

- The equivalent inductance of **series-connected** inductors is the sum of the individual inductances.



$$L_{eq} = L_1 + L_2 + \dots + L_N$$

- Voltage Divider Rule


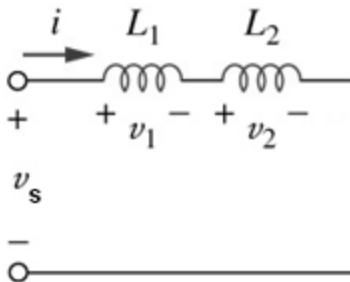


$$v_1 = \frac{L_1}{L_1 + L_2} v_s$$

$$v_2 = \frac{L_2}{L_1 + L_2} v_s$$

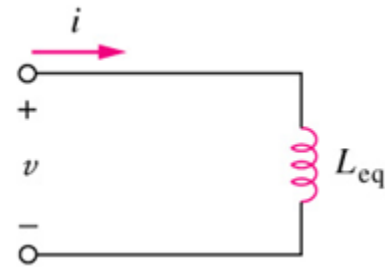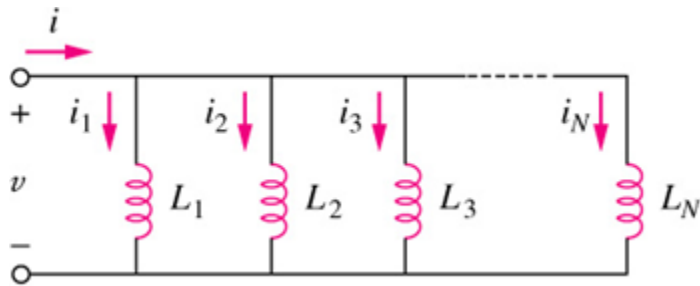
# Parallel Inductors

- The equivalent capacitance of **parallel** inductors is the reciprocal of the sum of the reciprocals of the individual inductances.



$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

- Current Divider Rule

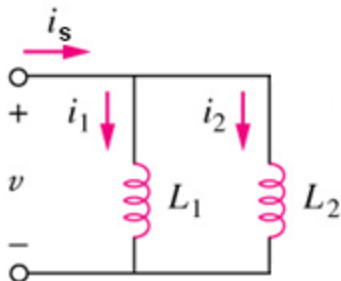

$$i_1 = \frac{L_2}{L_1 + L_2} i_s$$


$$i_2 = \frac{L_1}{L_1 + L_2} i_s$$



# Series and Parallel Inductor
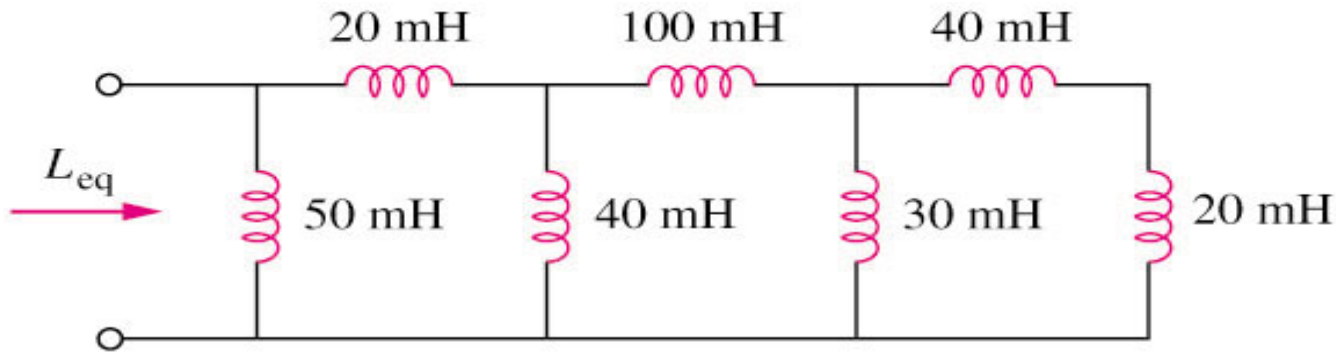
## Example 7



Calculate the equivalent inductance for the inductive ladder network in the circuit shown below:



**Answer:  $L_{eq} = \underline{25\text{mH}}$**

# Current and voltage relationship

- Current and voltage relationship for R, L, C
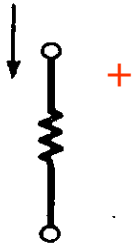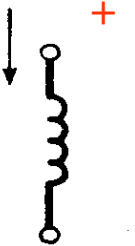
| Circuit element                                                                                    | Units             | Voltage                           | Current                           | Power                       |
|----------------------------------------------------------------------------------------------------|-------------------|-----------------------------------|-----------------------------------|-----------------------------|
| <br>Resistance    | ohms ( $\Omega$ ) | $v = Ri$<br>(Ohm's law)           | $i = \frac{v}{R}$                 | $p = vi = i^2 R$            |
| <br>Inductance   | henries (H)       | $v = L \frac{di}{dt}$             | $i = \frac{1}{L} \int v dt + k_1$ | $p = vi = Li \frac{di}{dt}$ |
| <br>Capacitance | farads (F)        | $v = \frac{1}{C} \int i dt + k_2$ | $i = C \frac{dv}{dt}$             | $p = vi = Cv \frac{dv}{dt}$ |