

# Electrical Science


## ENGR 2303

### Video 4

Dr. Mohamed Bingabr  
School of Engineering  
University of Central Oklahoma

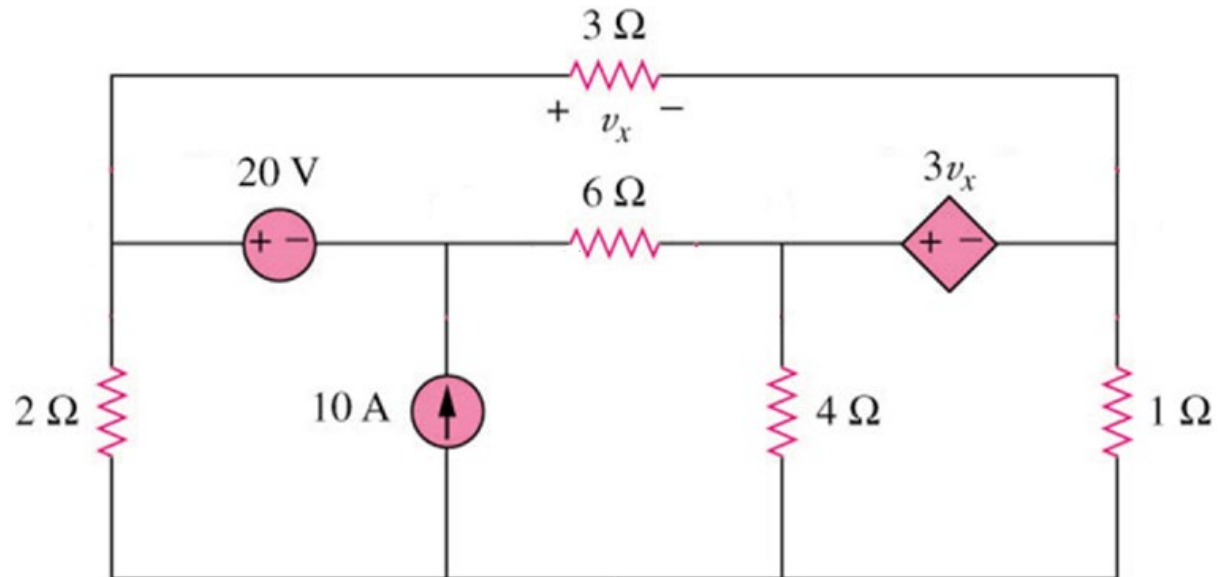
# Nodal Analysis

- Nodal analysis.
- Nodal analysis with dependent sources.
- Nodal analysis with voltage sources.
- Examples




# Nodal Analysis Steps

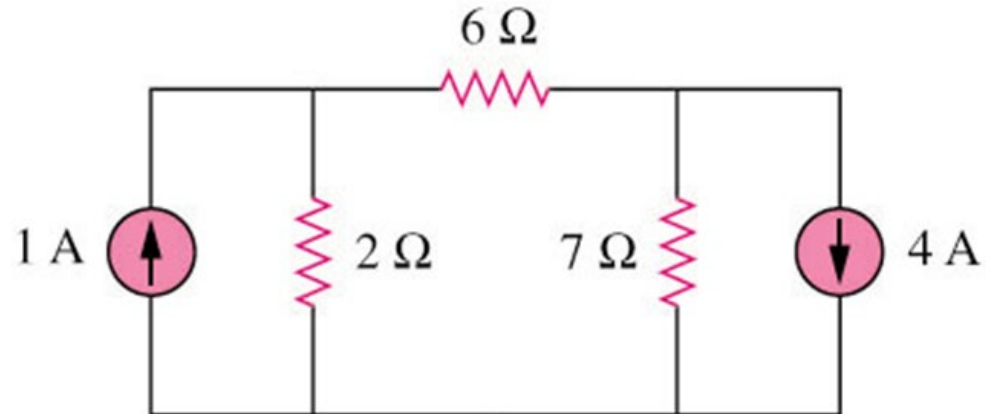1. Select a node as the reference node.
2. Assign voltages  $v_1, v_2, \dots, v_{n-1}$  to the remaining  $n-1$  nodes. The voltages are referenced with respect to the reference node.
3. Apply KCL to each of the  $n-1$  non-reference nodes. Use Ohm's law to express the branch currents in terms of node voltages.
4. Solve the resulting simultaneous equations to obtain the unknown node voltages.



# Nodal Analysis Example


Find the voltages across the resistors.

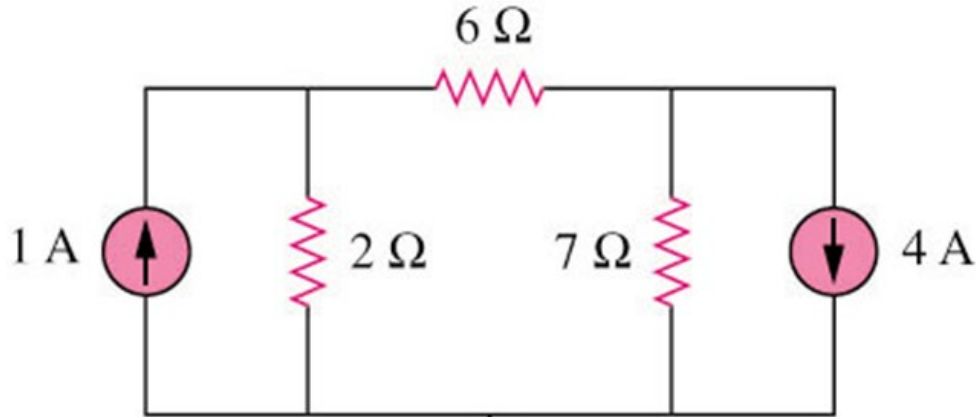

Answer  $v_1 = -2V$ ,  $v_2 = -14V$

# Nodal Analysis with Dependent source

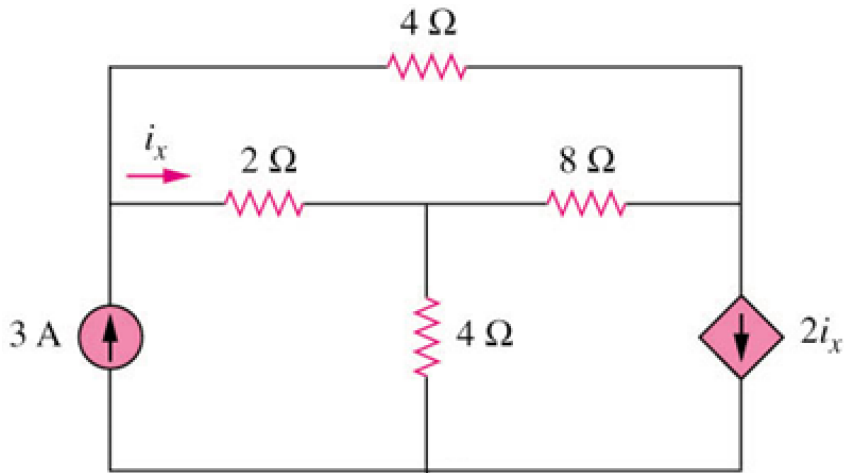
**Find the voltages and currents across the resistors.**



answer  $v_1 = 4.8\text{V}$ ,  $v_2 = 2.4\text{V}$ ,  $v_3 = -2.4\text{V}$


# Nodal Analysis with Voltage Source

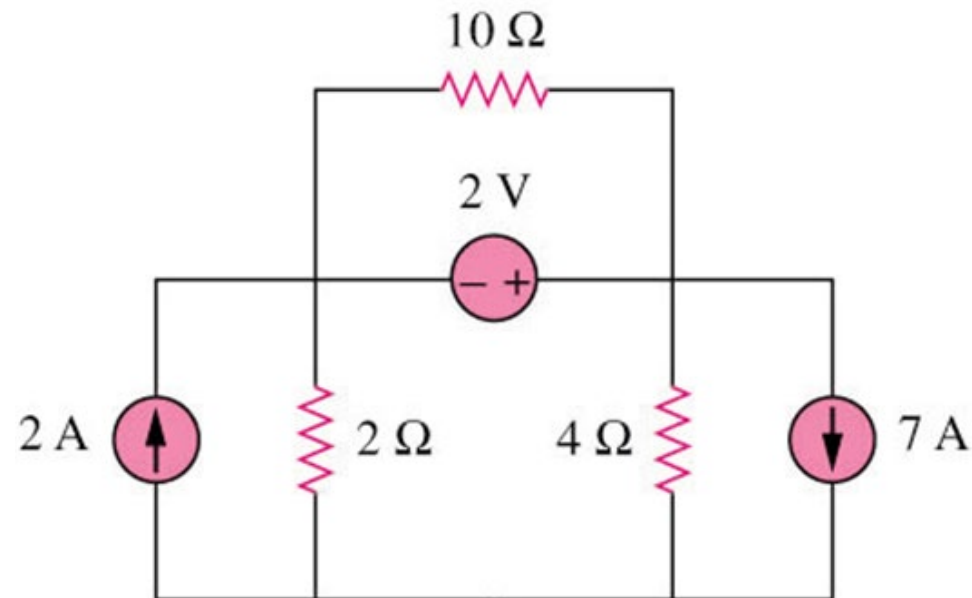1. Form a super-node by enclosing a voltage source connected between two non-reference nodes and any elements connected in parallel with it.
2. Take off all voltage sources in super-nodes and apply KCL to super-nodes.
3. Put voltage sources back to the nodes and apply KVL to relative loops.


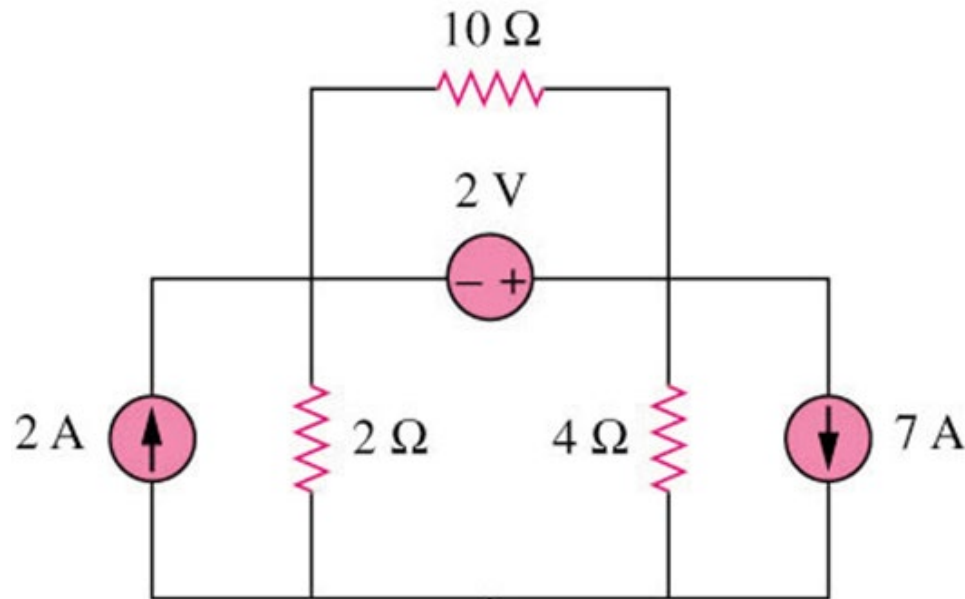
# Nodal Analysis with Voltage Source


Find the voltages and currents at the resistors



answer  $v_1 = -22/3$  V,  $v_2 = -16/3$  V

# Nodal Analysis with Independent Voltage Source

Find the voltages at the nodes

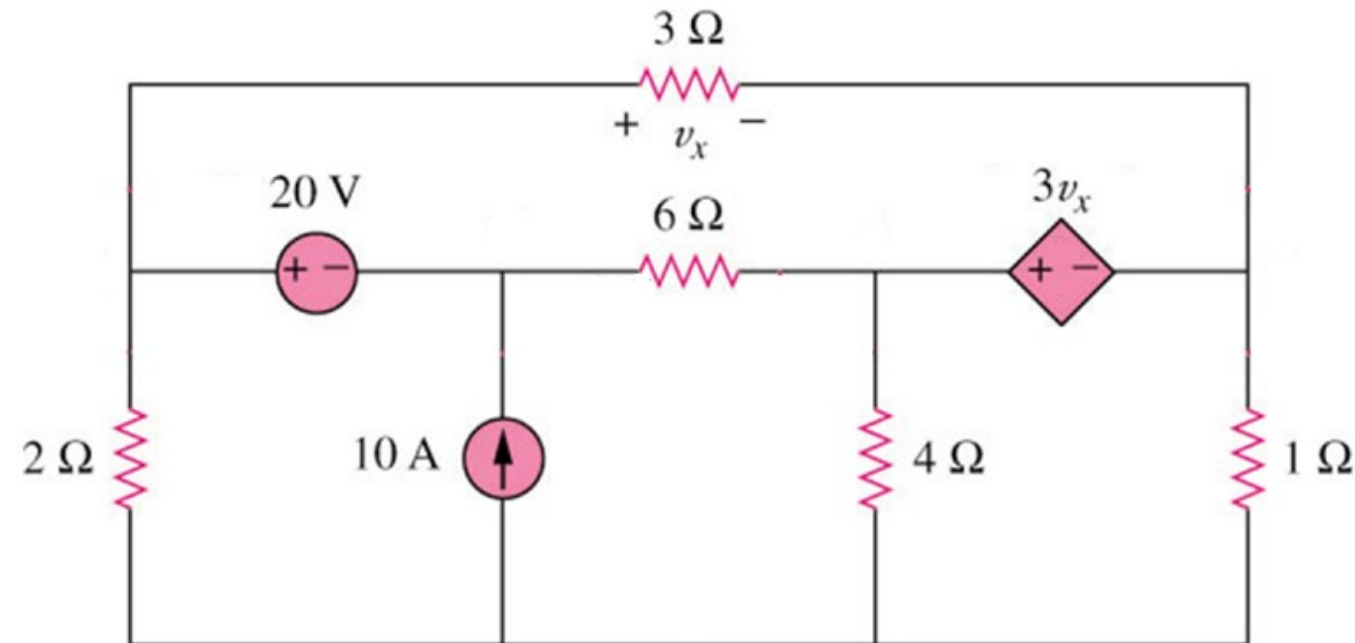

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 5 & 1 & -1 & -2 \\ 4 & 2 & -5 & -16 \\ -1 & 1 & 0 & 0 \\ 3 & 0 & -1 & -2 \end{bmatrix} \begin{bmatrix} 60 \\ 0 \\ -20 \\ 0 \end{bmatrix}$$



# Nodal Analysis with Inspection

By inspection, write the nodal voltage equations for the circuit

