


ENGR 2303 Electrical Science
Review Material for Test 4 (7/28/26 from 9-10:50 am)

The test will cover sinusoidal steady-state analysis


- Phasor relationships for circuit elements
- Impedance and admittance
- Kirchhoff's laws in the frequency domain
- Impedance combinations
- Nodal Analysis
- Mesh Analysis
- Superposition Theorem
- Source Transformation
- Thevenin and Norton Equivalent Circuits
- Op-Amp

Sample Questions

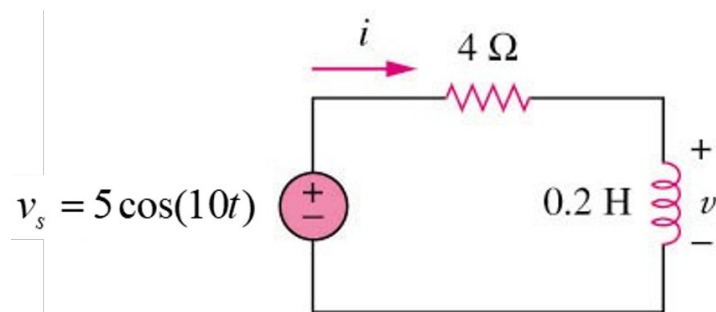
Q1) Refer to Figure below, determine $v(t)$ and $i(t)$.



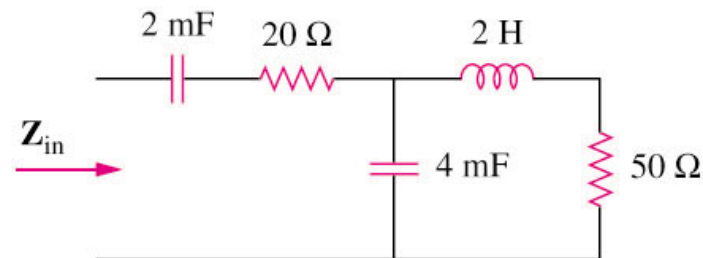
Q2) Determine the input impedance of the circuit in figure below at $\omega = 10$ rad/s.



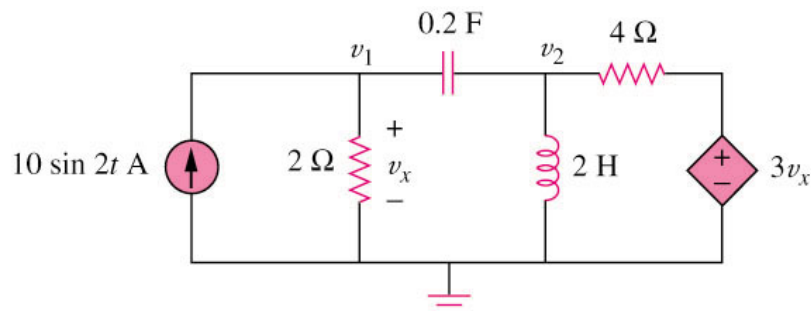
Q3) Using nodal analysis, find v_1 and v_2 in the circuit of figure below.



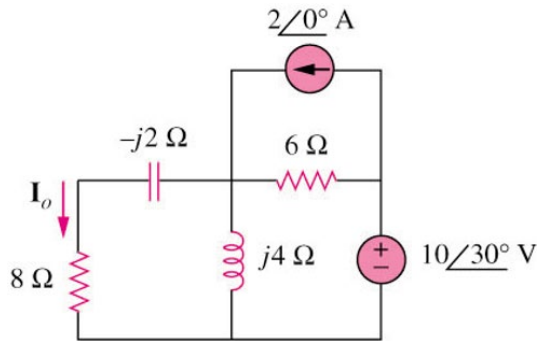
Q4) Find I_o in the following figure using mesh analysis.



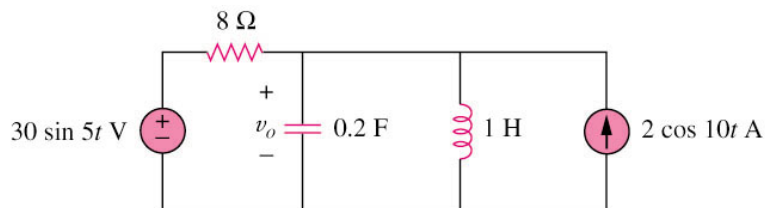
Q5) Calculate v_o in the circuit of figure shown below using the superposition theorem.



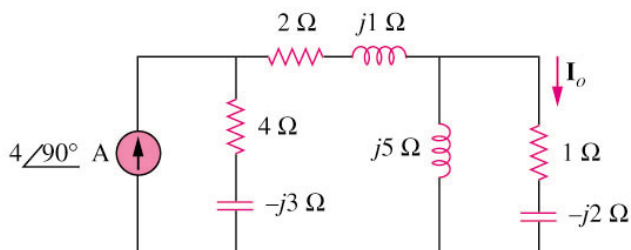Q6) Find I_o in the circuit of figure below using the concept of source transformation.



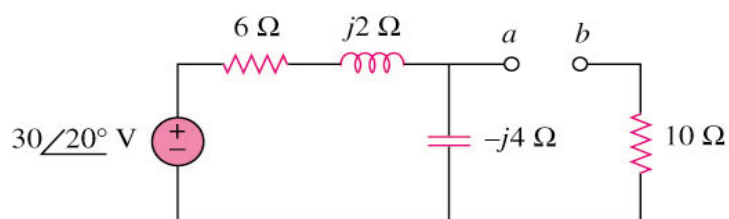Q7) Find the Thevenin equivalent at terminals a–b of the circuit below.



Q8) Evaluate the voltage gain $A_v = V_o/V_s$ in the op amp circuit. Find A_v at $\omega = 0$, $\omega \rightarrow \infty$, $\omega = 1/R_1C_1$, and $\omega = 1/R_2C_2$.

